


1) 50 MHz

choosing a counter

$$\begin{aligned} 2^{24} &= 16,777,216 \\ 2^{25} &= 33,554,432 \\ 2^{26} &= 67,108,864 \end{aligned}$$

But we only need $\frac{50 \text{ MHz}}{2} = 25 \text{ MHz}$
Since always (posedge clk)

 We can choose a 25 bit counter and use a "max" value constant of 25,000,000 to get 25MHz. Or rather, choose 24,999,999 or some similar value to avoid an incorrect reset,



PSUEDO CODE

```
module clockDiv(CLK, Rst, clkout)
```

```
  constants: MAX = 25,000,000
```

```
  register: [24:0] counter
```

```
  begin
```

```
    always at positive edge
```

```
      if Rst = 1
```

```
        counter = 0
```

```
        clkout = 0
```

```
      else if counter == 25,000,000
```

```
        counter = 0; clkout = !clkout
```