

Lab 08

Binary to Binary Coded Decimal

Category	Ryan Cruz ryan.cruz25@uga.edu	Zachary Davis zachdav@uga.edu
Pre-lab	50	50
In-lab Module & Testbench Design	50	50
In-lab Testbench Sim. & Analysis	50	50
In-lab FPGA Synthesis & Analysis	50	50
Lab Report Writing	50	50

November 8, 2017

Lab Purpose

The purpose of this lab is to improve the functionality of our previous lab in which we counted and displayed a 4-bit binary number as a hexadecimal number. In this lab, we will improve that design by displaying the 4-bit binary number as a two digit decimal number between 00 and 15. This can be accomplished by designing a Binary to Binary Coded Decimal Converter and a Multiplexed BCD Display Driver to display the output on the two 7-segment displays connected to the Spartan-3E FPGA.

Implementation Details

Display Driver

The purpose of this module is to properly display the UpDown value in Binary Coded Decimal using both seven segment digits.

Test Bench Code

```
'timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:
// Project Name:     Binary to Binary Coded Decimal
//
/////////////////////////////////////////////////////////////////
module Display_Driver_tb();
    reg Clk_s, Rst_s;
    reg [3:0] Tens_s;
    reg [3:0] Ones_s;
    wire A_s, B_s, C_s, D_s, E_s, F_s, G_s;
    wire Refresh_s;
    wire [3:0] DValue_s;
    wire Selector_s;

    Refresh Refresh_1 (Clk_s, Rst_s, Refresh_s, Selector_s);
    Mux2x1 Mux2x1_1 (Tens_s, Ones_s, Refresh_s, DValue_s);
    Seven_Segment_Display
    Seven_Segment_Display_1 (DValue_s, A_s, B_s, C_s, D_s, E_s, F_s, G_s);

    always
        begin
            Clk_s <= 1;
            #10;
```

```

                                Clk_s <= 0;
                                #10;

                                end

                                initial
                                begin
                                    Rst_s <= 1; Tens_s <= 4'b0000; Ones_s <= 4'b0000;
                                    #20;
                                    Rst_s<= 0; Tens_s <= 4'b0001; Ones_s <= 4'b0000;
                                    #50 $display ("DValue_s = %b", DValue_s);
                                    Rst_s<=0; Tens_s <= 4'b0001; Ones_s <= 4'b0001;
                                    #50 $display ("DValue_s = %b", DValue_s);
                                    Rst_s <= 0; Tens_s <= 4'b0001; Ones_s <= 4'b0011;
                                    #50 $display ("DValue_s = %b", DValue_s);
                                    Rst_s<=0; Tens_s <= 4'b0001; Ones_s <= 4'b0010;
                                    #50 $display ("DValue_s = %b", DValue_s);
                                    Rst_s<=0; Tens_s <= 4'b0000; Ones_s <= 4'b1111;
                                    #50 $display ("DValue_s = %b", DValue_s);
                                    Rst_s<=0; Tens_s <= 4'b0000; Ones_s <= 4'b1000;
                                    #50 $display ("DValue_s = %b", DValue_s);
                                    Rst_s<=0; Tens_s <= 4'b0000; Ones_s <= 4'b1010;
                                    #50 $display ("DValue_s = %b", DValue_s);

                                end
                                endmodule

```

Refresh

The purpose of this code is to refresh the two seven segment displays seperately and update the display seperetly.

Behavioral Module Code

```

'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:      Refresh
// Project Name:     Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module Refresh(Clk, Rst, Refresh, Selector);
    input Clk, Rst;

```

```

output reg Refresh, Selector;

parameter Divider = 2;
reg[19:0] Counter;
reg Clk_Count;

always @(posedge Clk) begin
    if( Rst == 1 )begin
        Counter <= 0;
        Refresh <= 0;
        Selector <=0;
        Clk_Count <= 0;
    end
    else begin
        if( Counter == Divider ) begin
            Refresh <= ~Clk_Count;
            Selector <= ~Clk_Count;
            Clk_Count <= ~Clk_Count;
            Counter <= 0;
        end
        else begin
            Refresh <= Clk_Count;
            Selector <= Clk_Count;
            Clk_Count <= Clk_Count;
            Counter <= Counter + 1;
        end
    end
end
endmodule

```

Test Bench Code

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:      Refresh
// Project Name:     Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module Refresh_tb();
    reg Clk_t, DivRst_t;
    wire Refresh_t, Selector_t;

```

```

Refresh Refresh_1(Clk_t, DivRst_t, Refresh_t, Selector_t);

always
    begin
        Clk_t <= 1;
        #10;
        Clk_t <= 0;
        #10;
    end

initial
begin
    DivRst_t <= 0;
    #100;
    DivRst_t <= 1;
    #200;
    DivRst_t <= 0;
end

endmodule

```

Binary to BCD

This is the actual module that converts the hexadecimal value to binary coded decimal by splitting it up into tens and ones. When ones reaches 10 it is reset to 0 and tens becomes one. The opposite occurs when counting down from 10 to 9.

Behavioral Module Code

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:      BinToBCD
// Project Name:     Binary to Binary Coded Decimal
//
/////////////////////////////////////////////////////////////////
module BinToBCD(Counter, Tens, Ones);
    input [3:0] Counter;
    output reg [3:0] Tens, Ones;

    always @ (Counter)
    begin

```

```

if (Counter == 4'b0000)
    begin
        Ones <= 4'b0000;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0001)
    begin
        Ones <= 4'b0001;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0010)
    begin
        Ones <= 4'b0010;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0011)
    begin
        Ones <= 4'b0011;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0100)
    begin
        Ones <= 4'b0100;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0101)
    begin
        Ones <= 4'b0101;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0110)
    begin
        Ones <= 4'b0110;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b0111)
    begin
        Ones <= 4'b0111;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b1000)
    begin
        Ones <= 4'b1000;
        Tens <= 4'b0000;
    end
else if (Counter == 4'b1001)
    begin

```

```

        Ones <= 4'b1001;
        Tens <= 4'b0000;
        end
    else if (Counter == 4'b1010)
        begin
            Ones <= 4'b0000;
            Tens <= 4'b0001;
            end
    else if (Counter == 4'b1011)
        begin
            Ones <= 4'b0001;
            Tens <= 4'b0001;
            end
    else if (Counter == 4'b1100)
        begin
            Ones <= 4'b0010;
            Tens <= 4'b0001;
            end
    else if (Counter == 4'b1101)
        begin
            Ones <= 4'b0011;
            Tens <= 4'b0001;
            end
    else if (Counter == 4'b1110)
        begin
            Ones <= 4'b0100;
            Tens <= 4'b0001;
            end
    else
        begin
            Ones <= 4'b0101;
            Tens <= 4'b0001;
            end
    end
endmodule

```

Test Bench Code

```

'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:       BinToBCD
// Project Name:      Binary to Binary Coded Decimal
//

```

```

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module BinToBCD_tb();
    reg [3:0] Count_t;
    wire [3:0] Tens_t;
    wire [3:0] Ones_t;

    BinToBCD BinToBCD_1(Count_t, Tens_t, Ones_t);

    initial begin
        Count_t <= 4'b0000;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0001;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0010;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0011;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0100;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0101;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0110;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b0111;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1000;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1001;
        #1 $display ("Ones_t = %b", Ones_t);
    end

```



```

        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1010;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1011;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1100;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1101;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1110;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);
        #10;
        Count_t <= 4'b1111;
        #1 $display ("Ones_t = %b", Ones_t);
        #1 $display ("Tens_t = %b", Tens_t);

    end
endmodule

```

UpDown

This module comes from a previous lab and still has the same behavior. It counts both up and down every rising clock edge depending on the state of UpDown and pauses when DivRst is high. It also resets back to 0 when Rst is high.

Behavioral Module Code

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:      UpDown
// Project Name:     Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module UpDown(Clk, Rst, Enable, UpDown, Count);

```

```

input Clk, Rst, Enable, UpDown;
output reg [3:0] Count = 4'b0000;

always @ (posedge Clk)
    begin
        if (Rst == 4'b0001)
            Count <= 4'b0000;
        else if (Enable == 4'b0000)
            Count <= Count;
        else
            begin
                if (UpDown == 4'b0001)
                    begin
                        if (Count == 4'b1111)
                            Count <= 4'b0000;
                        else
                            Count <= Count + 4'b0001;
                    end
                else
                    begin
                        if (Count == 4'b0000)
                            Count <= 4'b1111;
                        else
                            Count <= Count - 4'b0001;
                    end
            end
        end
    end
endmodule

```

Test Bench Code

```

'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:       UpDown
// Project Name:      Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module UpDown_tb();
    reg Clk_t, Rst_t, UpDown_t, Enable_t;
    wire [3:0] Count_t;

    UpDown UpDown_1(Clk_t, Rst_t, Enable_t, UpDown_t, Count_t);

```

```

initial
begin
    Clk_t <= 0;
    Rst_t <= 0;
    Enable_t <= 0;
    UpDown_t <= 0;
end

always
begin
    #10 Clk_t <= ~Clk_t;
end

initial
begin
    #5;
    UpDown_t <= 0; Rst_t <= 0; Enable_t <= 0;
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    #5;
    UpDown_t <= 1; Rst_t <= 0; Enable_t <= 1;
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    #5;
    UpDown_t <= 0; Rst_t <= 0; Enable_t <= 1;
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    #5;
    Enable_t <= 0;
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);
    #5;
    Enable_t <= 1;
    @(posedge Clk_t);
    @(posedge Clk_t);
    @(posedge Clk_t);

```

```

                @(posedge Clk_t);
                #5;
                Rst_t <= 1;
            end
        endmodule

```

Seven Segment Display

This module also comes from a previous lab and has the same behavior. It converts the input value from 0 to 15 to be displayed on a seven segment display by setting the appropriate LED segments to high to depict the value.

Behavioral Module Code

```

'timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:       Seven Segment Display
// Project Name:      Binary to Binary Coded Decimal
//
/////////////////////////////////////////////////////////////////
module Seven_Segment_Display(In, A, B, C, D, E, F, G);
    input [3:0] In;
    output reg A, B, C, D, E, F, G;

    always @ (In)
    begin
        if (In[3] == 0 && In[2] == 0 && In[1] == 0 && In[0] == 0)
            begin
                A <= 1;
                B <= 1;
                C <= 1;
                D <= 1;
                E <= 1;
                F <= 1;
                G <= 0;
            end
        else if (In[3] == 0 && In[2] == 0 && In[1] == 0 && In[0] == 1)
            begin
                A <= 0;
                B <= 1;
            end
    end
endmodule

```

```

        C <= 1;
        D <= 0;
        E <= 0;
        F <= 0;
        G <= 0;
    end
else if (In[3] == 0 && In[2] == 0 && In[1] == 1 && In[0] == 0)
begin
    A <= 1;
    B <= 1;
    C <= 0;
    D <= 1;
    E <= 1;
    F <= 0;
    G <= 1;
end
else if (In[3] == 0 && In[2] == 0 && In[1] == 1 && In[0] == 1)
begin
    A <= 1;
    B <= 1;
    C <= 1;
    D <= 1;
    E <= 0;
    F <= 0;
    G <= 1;
end
else if (In[3] == 0 && In[2] == 1 && In[1] == 0 && In[0] == 0)
begin
    A <= 0;
    B <= 1;
    C <= 1;
    D <= 0;
    E <= 0;
    F <= 1;
    G <= 1;
end
else if (In[3] == 0 && In[2] == 1 && In[1] == 0 && In[0] == 1)
begin
    A <= 1;
    B <= 0;
    C <= 1;
    D <= 1;
    E <= 0;
    F <= 1;
    G <= 1;
end
else if (In[3] == 0 && In[2] == 1 && In[1] == 1 && In[0] == 0)

```

```

begin
A <= 1;
B <= 0;
C <= 1;
D <= 1;
E <= 1;
F <= 1;
G <= 1;
end
else if (In[3] == 0 && In[2] == 1 && In[1] == 1 && In[0] == 1)
begin
A <= 1;
B <= 1;
C <= 1;
D <= 0;
E <= 0;
F <= 0;
G <= 0;
end
else if (In[3] == 1 && In[2] == 0 && In[1] == 0 && In[0] == 0)
begin
A <= 1;
B <= 1;
C <= 1;
D <= 1;
E <= 1;
F <= 1;
G <= 1;
end
else if (In[3] == 1 && In[2] == 0 && In[1] == 0 && In[0] == 1)
begin
A <= 1;
B <= 1;
C <= 1;
D <= 1;
E <= 0;
F <= 1;
G <= 1;
end
else if (In[3] == 1 && In[2] == 0 && In[1] == 1 && In[0] == 0)
begin
A <= 1;
B <= 1;
C <= 1;
D <= 0;
E <= 1;
F <= 1;

```

```

        G <= 1;
    end
else if (In[3] == 1 && In[2] == 0 && In[1] == 1 && In[0] == 1)
    begin
        A <= 0;
        B <= 0;
        C <= 1;
        D <= 1;
        E <= 1;
        F <= 1;
        G <= 1;
    end
else if (In[3] == 1 && In[2] == 1 && In[1] == 0 && In[0] == 0)
    begin
        A <= 1;
        B <= 0;
        C <= 0;
        D <= 1;
        E <= 1;
        F <= 1;
        G <= 0;
    end
else if (In[3] == 1 && In[2] == 1 && In[1] == 0 && In[0] == 1)
    begin
        A <= 0;
        B <= 1;
        C <= 1;
        D <= 1;
        E <= 1;
        F <= 0;
        G <= 1;
    end
else if (In[3] == 1 && In[2] == 1 && In[1] == 1 && In[0] == 0)
    begin
        A <= 1;
        B <= 0;
        C <= 0;
        D <= 1;
        E <= 1;
        F <= 1;
        G <= 1;
    end
else
    begin
        A <= 1;
        B <= 0;
        C <= 0;
    end

```

```

        D <= 0;
        E <= 1;
        F <= 1;
        G <= 1;
    end
end
endmodule

```

Test Bench Code

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:      Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:   13:43:37 10/30/2017
// Design Name:
// Module Name:    Seven Segment Display
// Project Name:   Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module Seven_Segment_Display_tb();
    reg [3:0] In_t;
    wire A_t, B_t, C_t, D_t, E_t, F_t, G_t;

    Seven_Segment_Display
    Seven_Segment_Display_1(In_t, A_t, B_t, C_t, D_t, E_t, F_t, G_t);

    initial
    begin
        //case 0
        In_t[3] <= 0; In_t[2] <= 0; In_t[1] <= 0; In_t[0] <= 0;
        #1 $display("A_t = %b", A_t);
        #1 $display("B_t = %b", B_t);
        #1 $display("C_t = %b", C_t);
        #1 $display("D_t = %b", D_t);
        #1 $display("E_t = %b", E_t);
        #1 $display("F_t = %b", F_t);
        #1 $display("G_t = %b", G_t);

        //case 1
        In_t[3] <= 0; In_t[2] <= 0; In_t[1] <= 0; In_t[0] <= 1;
        #1 $display("A_t = %b", A_t);
        #1 $display("B_t = %b", B_t);
        #1 $display("C_t = %b", C_t);
    end
endmodule

```



```

#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 2
In_t[3] <= 0; In_t[2] <= 0; In_t[1] <= 1; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 3
In_t[3] <= 0; In_t[2] <= 0; In_t[1] <= 1; In_t[0] <= 1;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 4
In_t[3] <= 0; In_t[2] <= 1; In_t[1] <= 0; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 5
In_t[3] <= 0; In_t[2] <= 1; In_t[1] <= 0; In_t[0] <= 1;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 6
In_t[3] <= 0; In_t[2] <= 1; In_t[1] <= 1; In_t[0] <= 0;

```

```

#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 7
In_t[3] <= 0; In_t[2] <= 1; In_t[1] <= 1; In_t[0] <= 1;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 8
In_t[3] <= 0; In_t[2] <= 0; In_t[1] <= 0; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 0
In_t[3] <= 1; In_t[2] <= 0; In_t[1] <= 0; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 9
In_t[3] <= 1; In_t[2] <= 0; In_t[1] <= 0; In_t[0] <= 1;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

```

```

//case 10
In_t[3] <= 1; In_t[2] <= 0; In_t[1] <= 1; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 11
In_t[3] <= 1; In_t[2] <= 0; In_t[1] <= 1; In_t[0] <= 1;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 12
In_t[3] <= 1; In_t[2] <= 1; In_t[1] <= 0; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 13
In_t[3] <= 1; In_t[2] <= 1; In_t[1] <= 0; In_t[0] <= 1;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);
#1 $display("E_t = %b", E_t);
#1 $display("F_t = %b", F_t);
#1 $display("G_t = %b", G_t);

//case 14
In_t[3] <= 1; In_t[2] <= 1; In_t[1] <= 1; In_t[0] <= 0;
#1 $display("A_t = %b", A_t);
#1 $display("B_t = %b", B_t);
#1 $display("C_t = %b", C_t);
#1 $display("D_t = %b", D_t);

```

```

        #1 $display("E_t = %b", E_t);
        #1 $display("F_t = %b", F_t);
        #1 $display("G_t = %b", G_t);

        //case 15
        In_t[3] <= 1; In_t[2] <= 1; In_t[1] <= 1; In_t[0] <= 1;
        #1 $display("A_t = %b", A_t);
        #1 $display("B_t = %b", B_t);
        #1 $display("C_t = %b", C_t);
        #1 $display("D_t = %b", D_t);
        #1 $display("E_t = %b", E_t);
        #1 $display("F_t = %b", F_t);
        #1 $display("G_t = %b", G_t);

    end
endmodule

```

Clock Divider

This as well comes from a previous lab and allows you to reduce a 50mHz clock cycle to anything lower than that by choosing the correct divider value. We used 25 million to output a 1 Hz clock cycle from this project.

Behavioral Module Code

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:      Clock Divider
// Project Name:     Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module Clock_Divider(Clk_In, Div_Rst, Clk_Out);
    input Clk_In, Div_Rst;
    output reg Clk_Out;
    reg [24:0] counter;

    always @(posedge Clk_In or posedge Div_Rst)
        begin
            if (Div_Rst == 1'b1)
                begin

```

```

        counter <= 0;
        Clk_Out <= 0;
        end
    else
        begin
            counter <= counter + 1;
            if (counter == 25_000_000) //Set to 5 to see behavior in sim.
                begin
                    counter <= 0;
                    Clk_Out <= ~Clk_Out;
                    end
                end
            end
        end
    end
endmodule

```

Test Bench Code

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:      Clock Divider
// Project Name:     Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
module Clock_Divider_tb();
    reg Clk_In_t, Div_Rst_t;
    wire Clk_Out_t;

    Clock_Divider Clock_Divider_1(Clk_In_t, Div_Rst_t, Clk_Out_t);

    always
        begin
            Clk_In_t <= 1;
            #10;
            Clk_In_t <= 0;
            #10;
        end

    initial begin
        Div_Rst_t <= 0;
        #5;
    end
endmodule

```

```

                Div_Rst_t <= 1;
                #5;
                Div_Rst_t <= 0;
            end
        endmodule

```

Top Module

This is the Top Module that calls all the previous modules and links them all together so that we can implement our coded on the Spartan3E and see the desired behavior.

Behavioral Module Code

```

'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////
// Company:          Zachary Davis & Ryan Cruz
// Engineer:
//
// Create Date:      13:43:37 10/30/2017
// Design Name:
// Module Name:
// Project Name:     Binary to Binary Coded Decimal
//
////////////////////////////////////////////////////////////////
module TopModule(Clk, DivRst, Rst, UpDown, Enable, A, B, C, D, E, F, G, Selector);
    input Clk, DivRst, Rst, UpDown, Enable;
    output A, B, C, D, E, F, G, Selector;

    wire ClkOut;
    wire [3:0] Count;
    wire [3:0] Tens, Ones;

    Clock_Divider Clock_Divider_1(ClkIn, DivRst, ClkOut);
    UpDown UpDown_1(ClkOut, Rst, Enable, UpDown, Count);
    BinToBCD BinToBCD_1(Count, Tens, Ones);
    Display_Driver
    Display_Driver_1(Clk, Rst, Tens, Ones, A, B, C, D, E, F, G, Selector);

endmodule

```


UCF

This maps all the correct switches and buttons to those on the board as well as the clock to oscillator.

```
NET "Clk" LOC = "C9";
NET "Rst" LOC = "K17" | PULLDOWN;
NET "DivRst" LOC = "D18" | PULLDOWN;
NET "Enable" LOC = "N17";
NET "UpDown" LOC = "H18";
NET "A" LOC = B4;
NET "B" LOC = A4;
NET "C" LOC = D5;
NET "D" LOC = C5;
NET "E" LOC = A6;
NET "F" LOC = B6;
NET "G" LOC = E7;
NET "Selector" LOC = F7;
```


Experimental Results

Waveforms

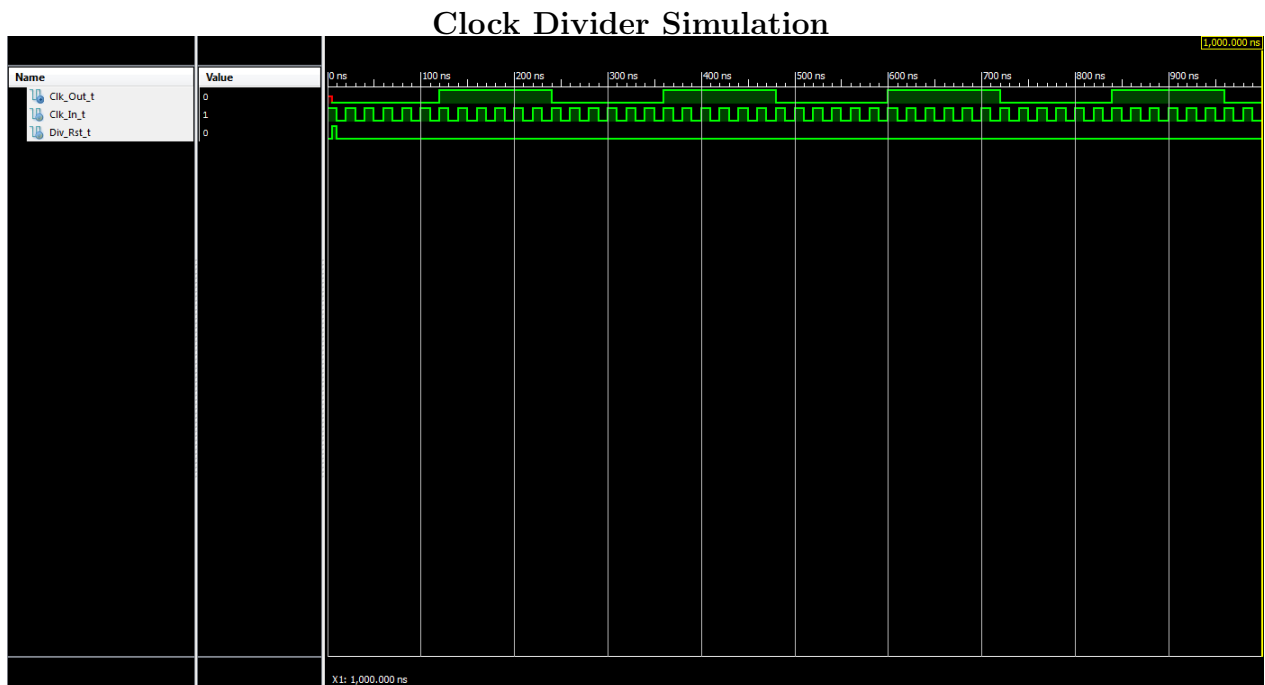


This waveform shows dividing the Sparten3E's 50mHz clock cycle into a 5mHz clock cycle by using a divider of 5. We did this so we could see the tested behavior in the sim. To achieve 1mHz we will use a divider of 25 million in the actual implementation.

2x1 Multiplexor Simulation

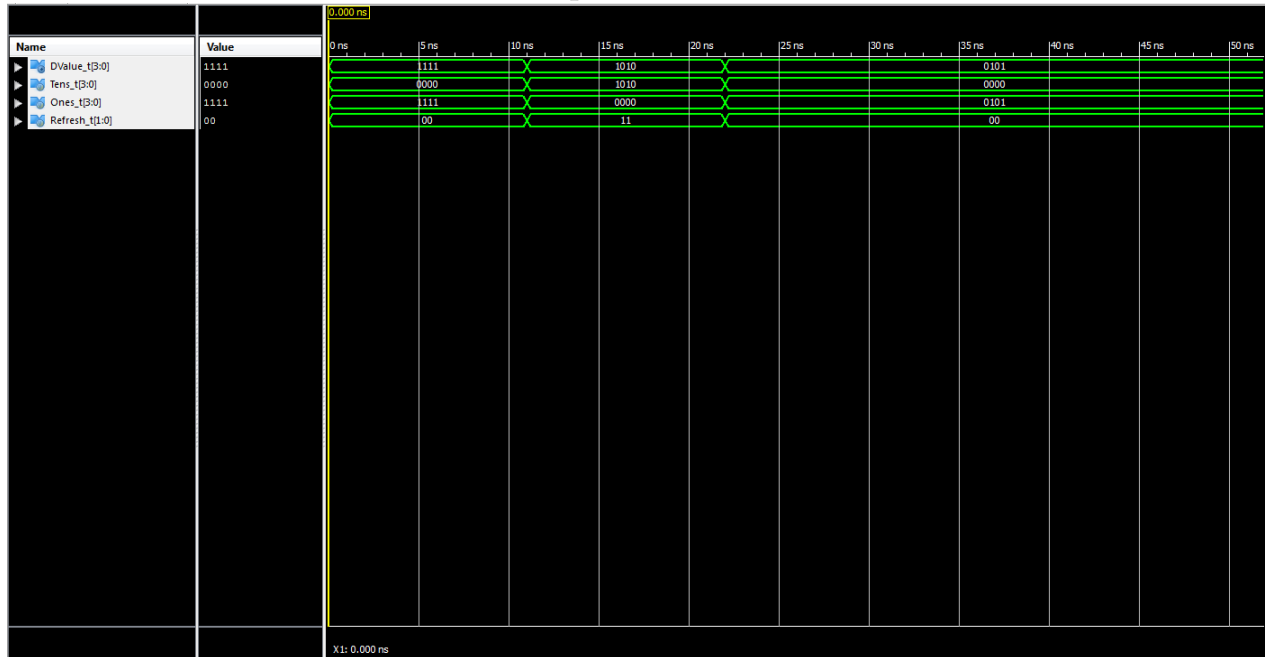


This waveform shows how the multiplexor will output the tens value of the ones value based on the state of refresh. The values used are not realistic but rather just used to show that the logic of the module works.

Refresh Simulation

 


This waveform shows how the value of DivRst and Refresh act on Selector or the value that determines the display digit. When refresh is high selector is high and the tens digits is refreshed. When refresh is low the ones digit is refreshed. Finally when DivRst is high the current state hold until DivRst is low again.

UpDown Simulation

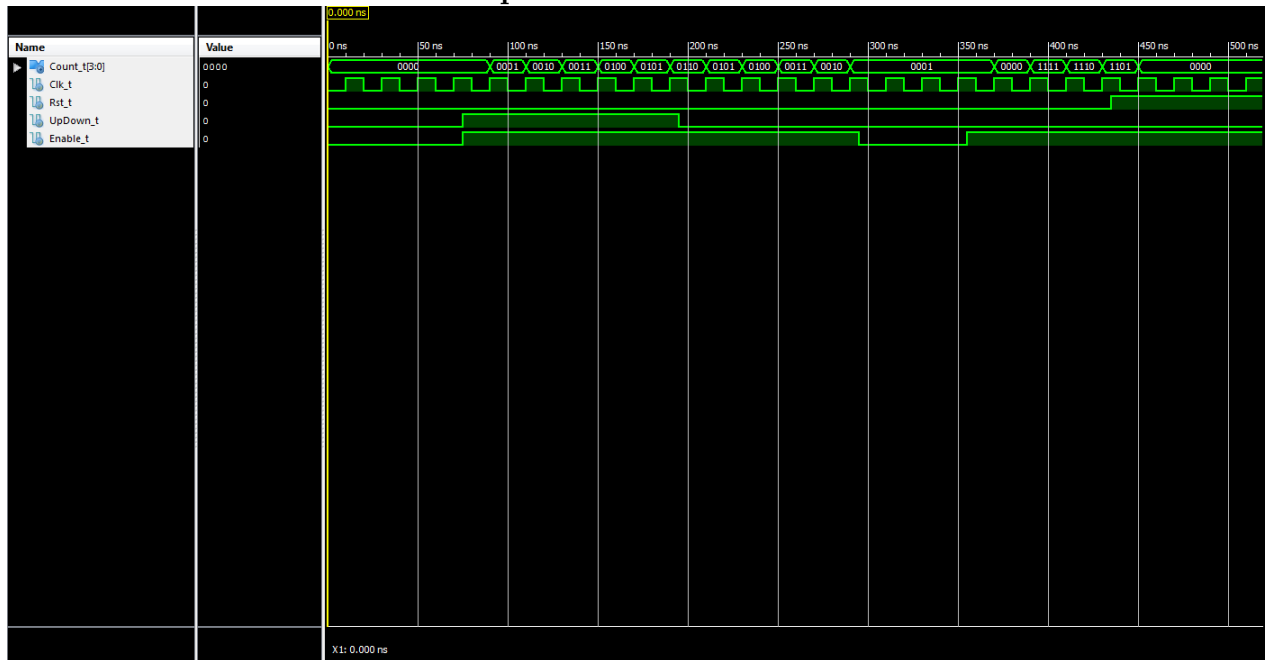


This is from a previous lab and show the behavior of UpDown. When Enable is low or DivRst is high the current state is held until the opposite of each of those values. If UpDown is high the values are counted up and wrap around. The opposite is true when UpDown is low. Finally if reset is high it returns to the 0 state.

Seven Segment Display Simulation

 

This waveform shows how the actual value is mapped to the seven-segment display. The value of `In` is the number that we wish to display, and the values of `A-G` are set high when we want that LED segment on. We combine these LEDs to display certain numbers, and that is shown in the waveform.

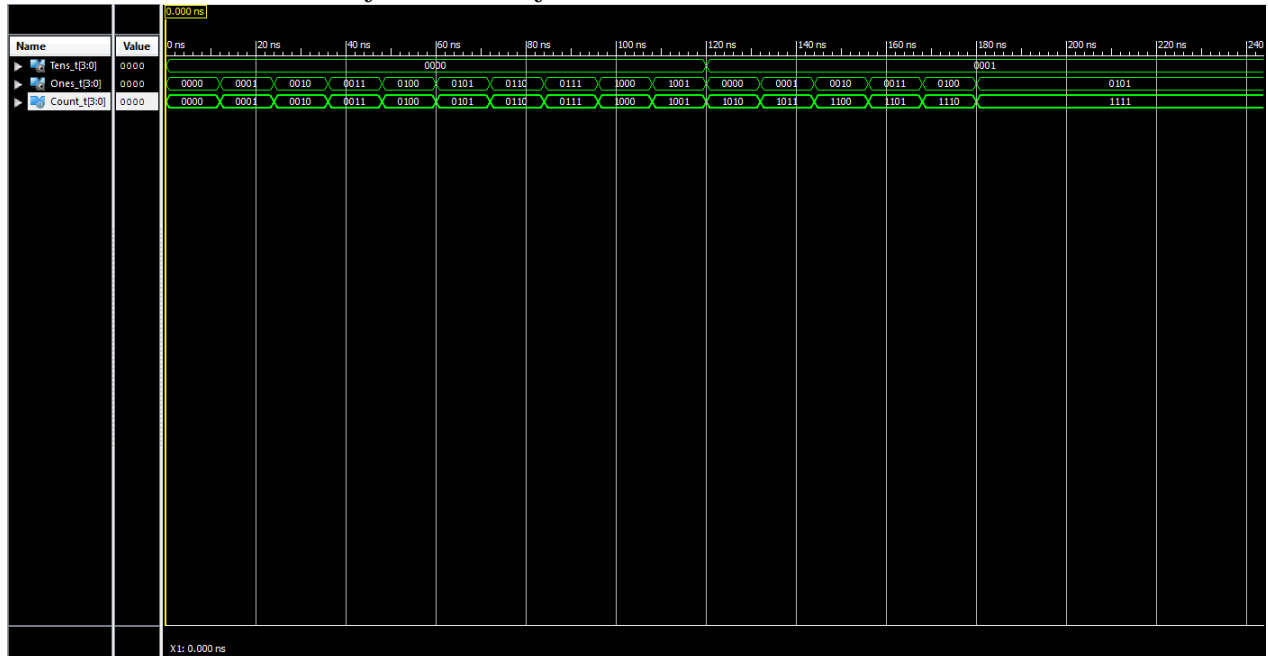Binary To Binary Coded Decimal Simulation



This waveform simulates the way that binary coded decimal is supposed to work. The counter is split into two variables or two digits. When ones counts up to 10 it is reset to 0 and tens is increased to one. When Ones counts down from 0 tens is decreased to 0 and ones is set to nine. All other behavior is that same from previous labs counting in Hex.

Significance

The introduction of the Binary Coded Decimal and Refresher features add a great deal of human readability and simplicity to the physical implementation, and overall improve the UpDown design. Binary Coded Decimal translation is a very useful technique that is used across several areas of computer systems when displaying a number is needed. The same goes for the display driver that we implemented. Whether 7-segment displays or other LED screens, knowing the digital design behind it is very useful and important.

Comments/Suggestions

The lab was a nice, natural extension of UpDown. The lab demo requirements seemed clear up until the actual demo, when we had one large testbench file, according to the “Demo the overall module testbench waveform...” instruction, and we were actually supposed to have separate testbenches for each module. This turned out to not be a problem since we had just enough time to implement them, except for the Refresher module, which was working great on the board, but not on the testbench, and it was not explicitly mentioned in the Lab Demo requirements, as said before.